
Table of Contents

.....	1
Question 1 + Question 2	1
Question 3	1
Question 4a	6
Question 4b	6
Question 4d	6
Question 5	12

```
clear
clc
```

Question 1 + Question 2

I do not want mistakes from my incomplete Assingmnet 3 to affect this to carry over. R3 was set to 10.

Question 3

```
R1 = 1;
R2 = 2;
C = 0.25;
L = 0.2;
alpha = 100;
R4 = 0.1;
R3 = 10;
Ro = 1000;

G = [
    1    0    0    0    0    0    0;
   -1/R2 (1/R1)+(1/R2)  -1    0    0    0    0;
    0    1    0   -1    0    0    0;
    0    0   -1   1/R3    0    0    0;
    0    0    0    0  -alpha    1    0;
    0    0    0   1/R3   -1    0    0;
    0    0    0    0    0  -1/R4 (1/R4)+(1/Ro)];

C_Mat = [
    0    0    0    0    0    0    0;
   -C    C    0    0    0    0    0;
    0    0   -L    0    0    0    0;
    0    0    0    0    0    0    0;
    0    0    0    0    0    0    0;
    0    0    0    0    0    0    0;
    0    0    0    0    0    0    0];

% V = [V2; V1; I1; V3; I3; V4; Vo]
```

```

%i DC Sweep
Vin = linspace(-10,10,100);
Vo = zeros(100,1);
V3 = zeros(100,1);

for i = 1:100
    F=[Vin(i); 0; 0; 0; 0; 0; 0];
    V = G\F;
    Vo(i) = V(7);
    V3(i) = V(4);
end

figure(1)
plot(Vin,Vo)
title('Vin vs Vout')
xlabel('Vin (V)')
ylabel('Vout(V)')

figure(2)
plot(Vin,V3)
title('Vin vs V3')
xlabel('Vin (V)')
ylabel('V3 (V)')

%ii AC Sweep

omega = linspace(1,1E4,10000);
Vin = 1;
Vo = zeros(10000,1);
F=[Vin; 0; 0; 0; 0; 0; 0];
for i = 1:1000
    V = (G +(omega(i)*2*pi*C_Mat *1j)) \F;
    Vo(i) = V(7);
end

figure(3)
semilogx(omega,Vo)
title('Omega vs Vout')
xlabel('omega')
ylabel('Vout(V)')

gain = 20*log10(abs(Vo/Vin));
figure(4)
semilogx(omega,gain)
title('Omega vs gain')
xlabel('Vin (V)')
ylabel('Vout(V)')

%iii AC Sweep2 (with random perturbations on C)

omeega = pi;

for i = 1:10000

```

```


C_dist = normrnd(C,0.05);
C_Mat = [
    0 0 0 0 0 0 0;
    -C_dist C_dist 0 0 0 0 0;
    0 0 -L 0 0 0 0;
    0 0 0 0 0 0 0;
    0 0 0 0 0 0 0;
    0 0 0 0 0 0 0;
    0 0 0 0 0 0 0];



V = (G +(omega(i)*2*pi*C_Mat *1j)) \F;
Vo(i) = V(7);
end



gain = 20*log(abs(Vo/Vin));
figure(5)
histogram(gain)
title('Gain with Capacitor Noise')
xlabel('Gain (dB)');

```

Warning: Imaginary parts of complex X and/or Y arguments ignored

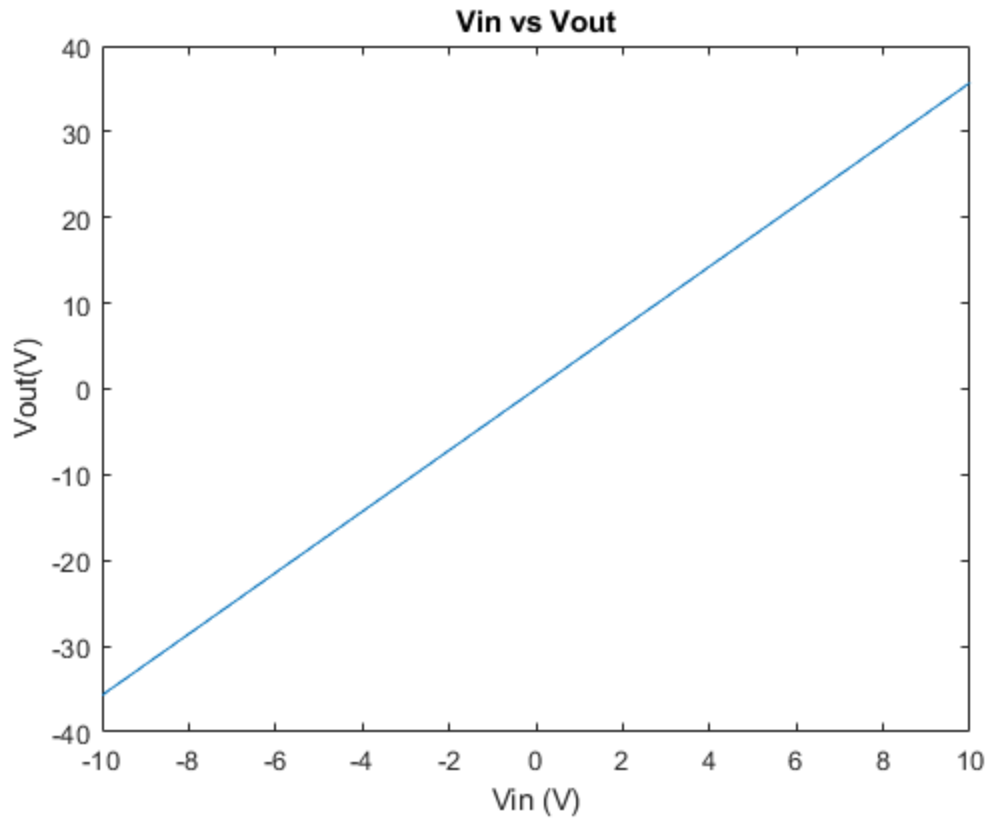

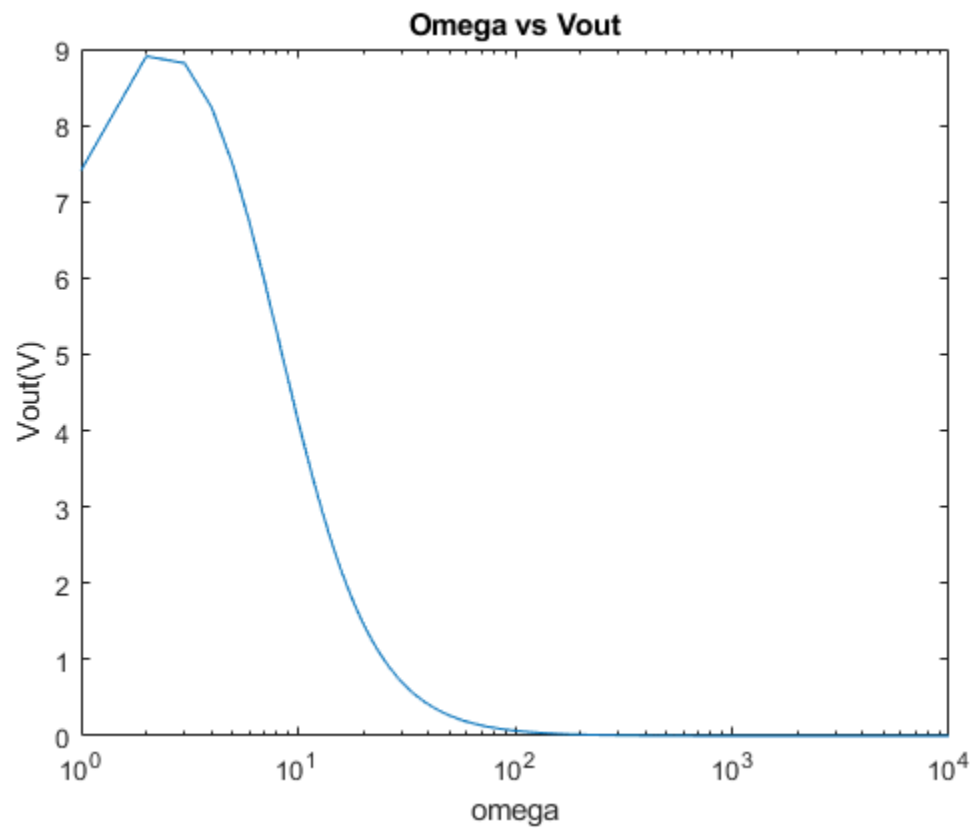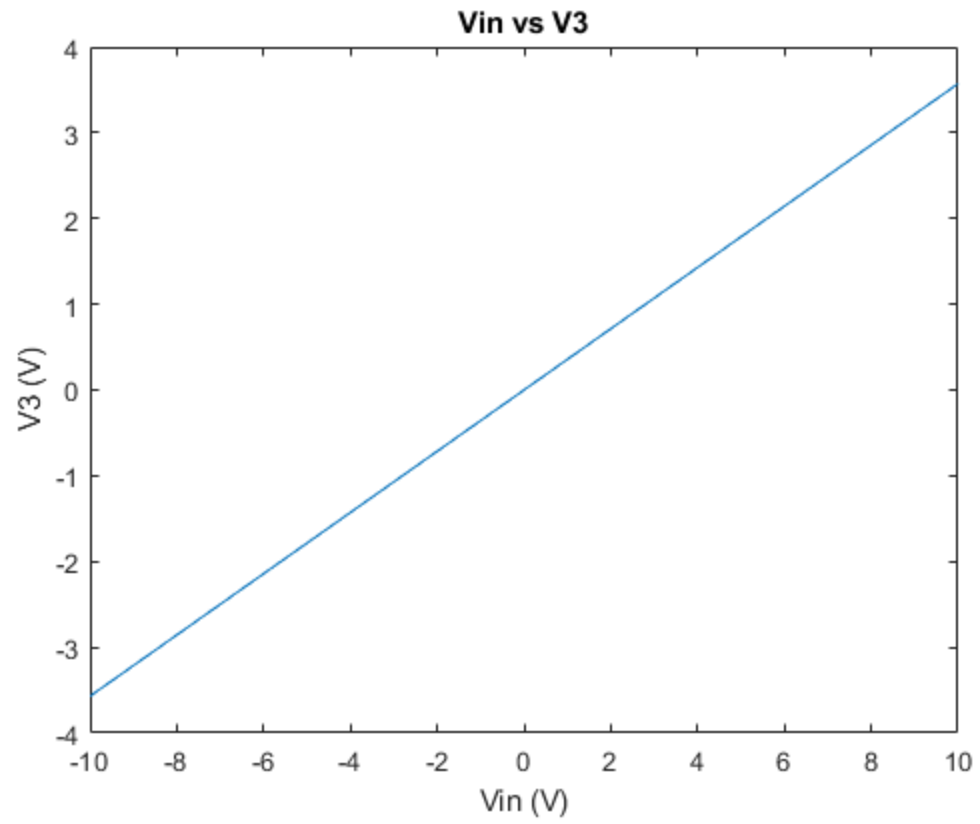

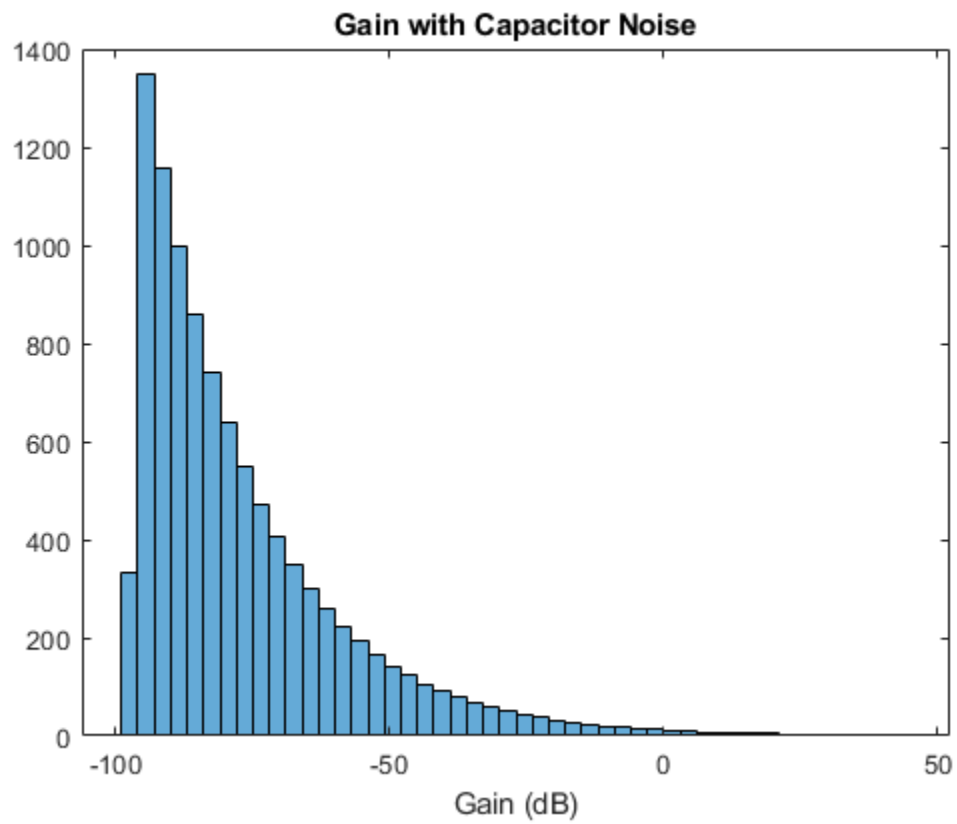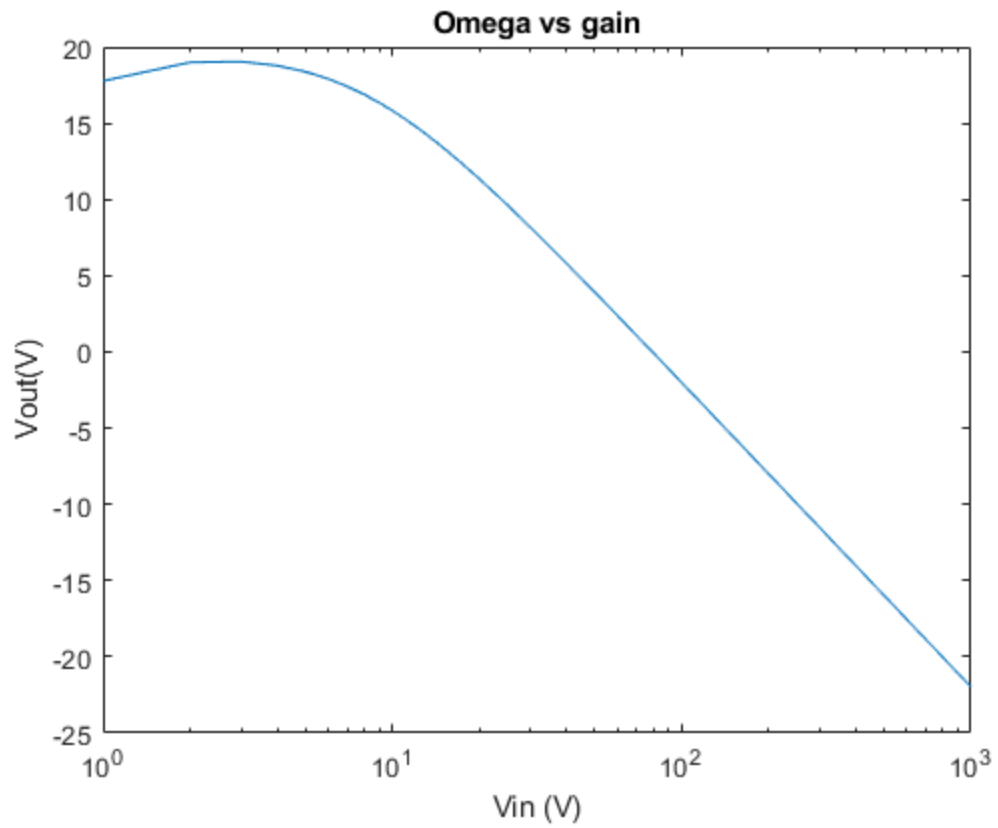

Question 4a

An RLC Circuit

Question 4b

The capacitance and inductance in the circuit are affected by the frequency. As the frequency is increased, the impedance of the capacitor (Z_c) decreases, while the impedance of the Inductor (Z_l) Increases.

Question 4d

Finite difference solution in the Time Domain:

```
simulation_time = 1000; % run simulation for 1 second
dt = 1; % time step

inputA = zeros(1,1000);
Vpre = zeros(7,1); %V(i-1)
% start simulation
for time = dt:dt:simulation_time

    % input A: step that transitions from 0 to 1 at t=0.03s
    if time < 30
        input_A(1,time) = 0;
    else
        input_A(1,time) = 1;
    end

    F =[input_A(1,time); 0; 0; 0; 0; 0; 0; 0];

    Vout = (G +C)\ (C.*Vpre) + F;
    Vout1_store(1,time) = Vout(7);

    Vpre = Vout;
end

Time = linspace(dt,simulation_time,simulation_time);

figure(6)
plot(Time,input_A)
hold on;
plot(Time,abs(Vout1_store))
xlim([0 1000])
ylim([0 1.2])
xlabel('Time (ms)')
ylabel('Voltage(V)')
hold off
legend('Vin','Vout')

% input B: sin(2*pi*f t) function with f = 1/(0.03)
input_B = zeros(1,1000);
```

```

Vpre = zeros(7,1); %V(i-1)
f = 1/30;

% start simulation
for time = dt:dt:simulation_time

    input_B(time) = sin(2*pi*f*time);

    F=[input_B(1,time); 0; 0; 0; 0; 0; 0];

    Vout = (G +C)\ (C.*Vpre) + F;
    Vout2_store(1,time) = Vout(7);

    Vpre = Vout;
end

Time = linspace(dt,simulation_time,simulation_time);

figure(7)
plot(Time,input_B)
hold on;
plot(Time,abs(Vout2_store))
xlim([0 100])
ylim([-1.1 1.1])
xlabel('Time (ms)')
ylabel('Voltage(V)')
hold off
legend('Vin','Vout')

% input C: A gaussian pulse with a magnitude of 1, std dev. of 0.03s
% and a delay of 0.06s
input_C = zeros(1,1000);

% start simulation
for time = dt:dt:simulation_time

    input_C(1,time) = (exp(-2*log(2)*(time-60).^2/
(30)^2)).*cos(-2*pi*f*(time-60));

    F=[input_C(1,time); 0; 0; 0; 0; 0; 0];

    Vout = (G +C)\ (C.*Vpre) + F;
    Vout3_store(1,time) = Vout(7);

    Vpre = Vout;
end

Time = linspace(dt,simulation_time,simulation_time);

figure(8)
plot(Time,input_C)
hold on;

```

```

    plot(Time,abs(Vout3_store))
    xlim([0 200])
    % ylim([-1.1 1.1])
    xlabel('Time (ms)')
    ylabel('Voltage(V)')
    hold off
    legend('Vin','Vout')

% Frequency Plots
A_fin = fftshift(fft(input_A));
B_fin = fftshift(fft(input_B));
C_fin = fftshift(fft(input_C));

A_fout = fftshift(fft(Vout1_store));
B_fout = fftshift(fft(Vout2_store));
C_fout = fftshift(fft(Vout3_store));



figure(9)
plot(Time,A_fin)
hold on
plot(Time,A_fout)
hold off
title('Fourier Transform: Step Input')
xlabel('Frequency')
ylabel('Magnitude')
legend('Input','Output')



figure(10)
plot(Time,B_fin)
hold on
plot(Time,B_fout)
hold off
title('Fourier Transform: Sine Wave Input')
xlabel('Frequency')
ylabel('Magnitude')
legend('Input','Output')



figure(11)
plot(Time,C_fin)
hold on
plot(Time,C_fout)
hold off
title('Fourier Transform: Gaussian Pulse Input')
xlabel('Frequency')
ylabel('Magnitude')
legend('Input','Output')

Warning: Imaginary parts of complex X and/or Y arguments ignored
Warning: Imaginary parts of complex X and/or Y arguments ignored
Warning: Imaginary parts of complex X and/or Y arguments ignored
Warning: Imaginary parts of complex X and/or Y arguments ignored
Warning: Imaginary parts of complex X and/or Y arguments ignored
Warning: Imaginary parts of complex X and/or Y arguments ignored

```

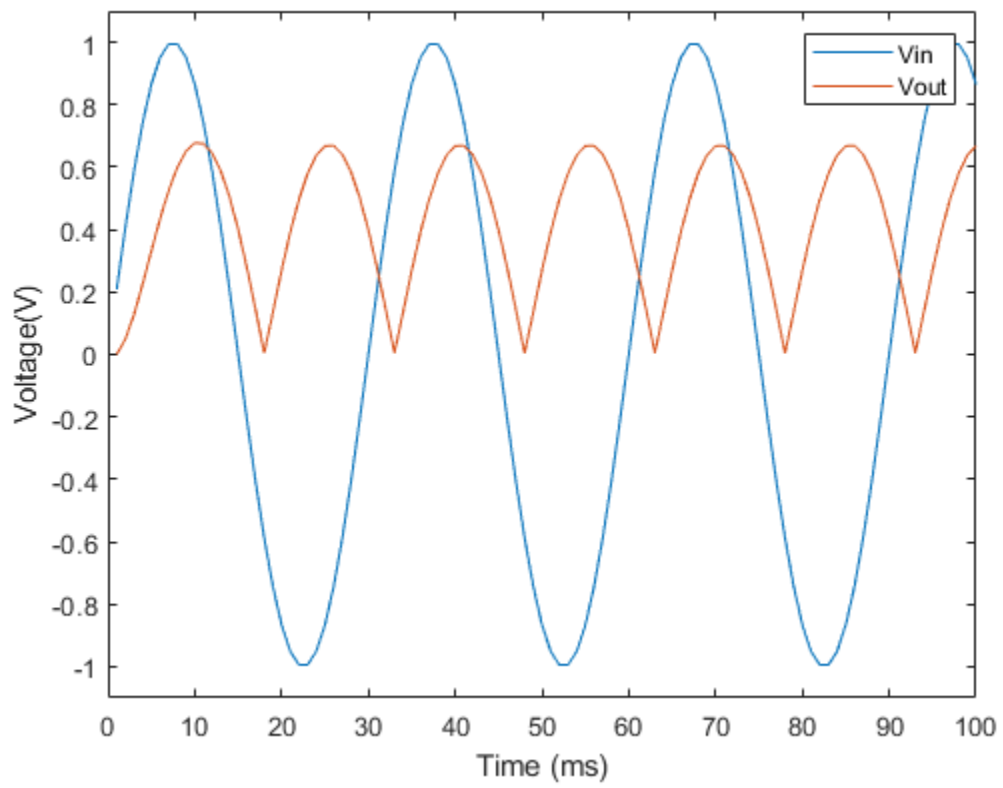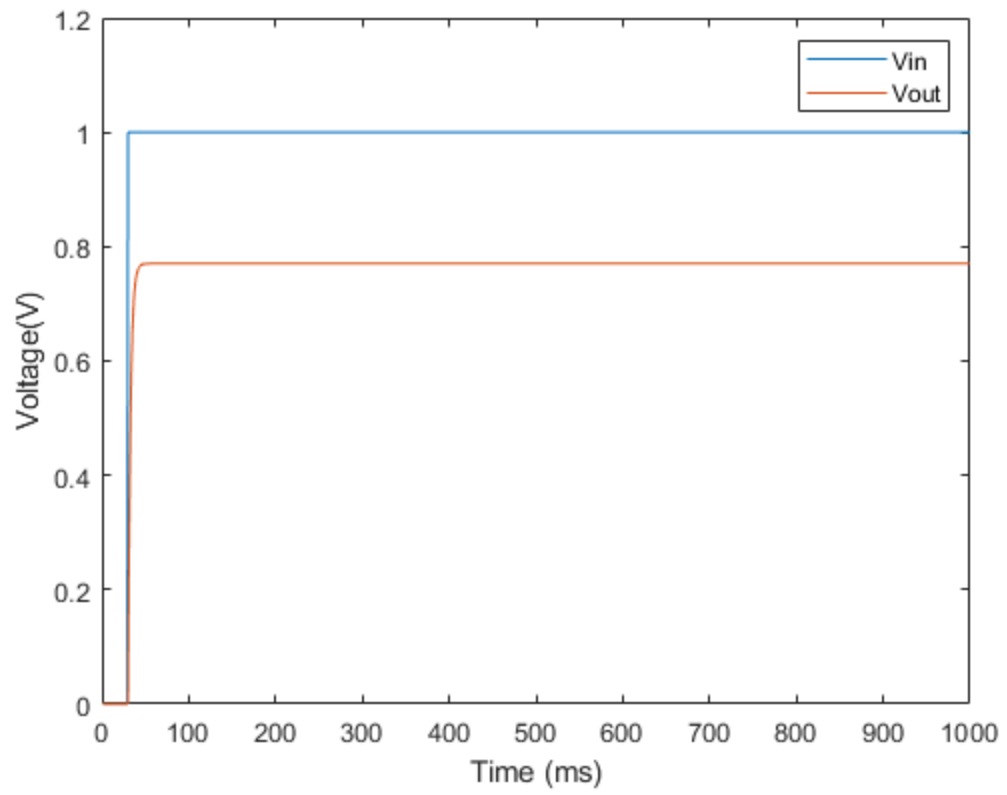

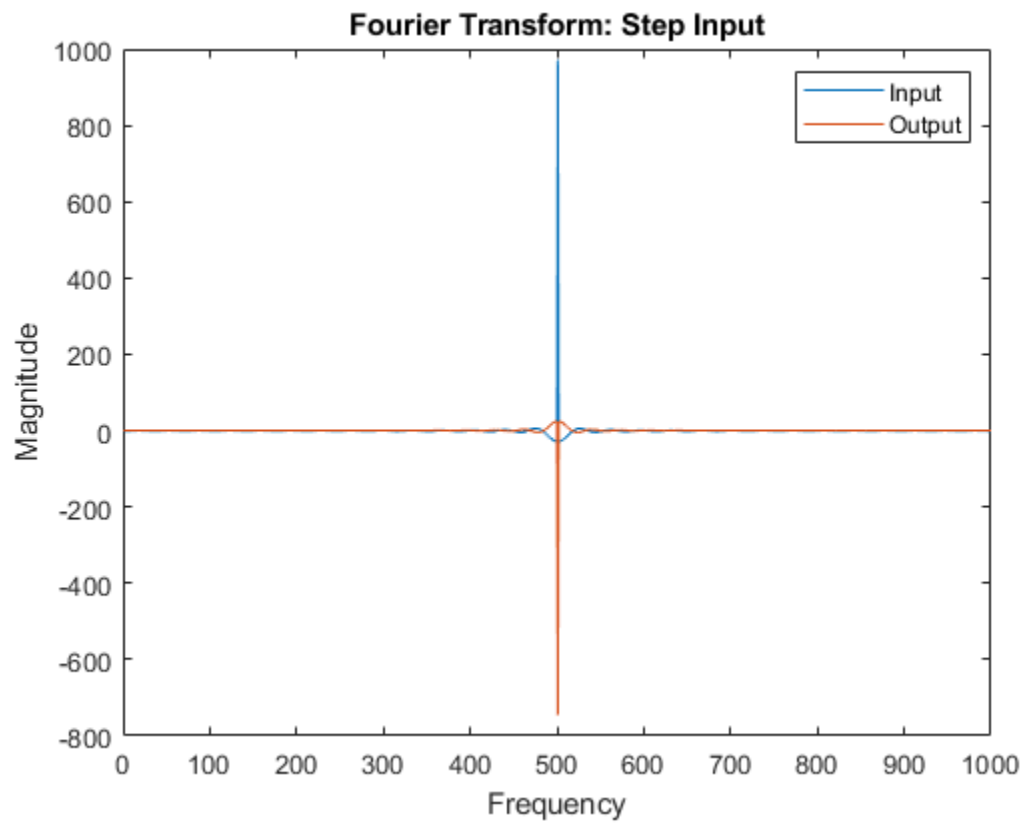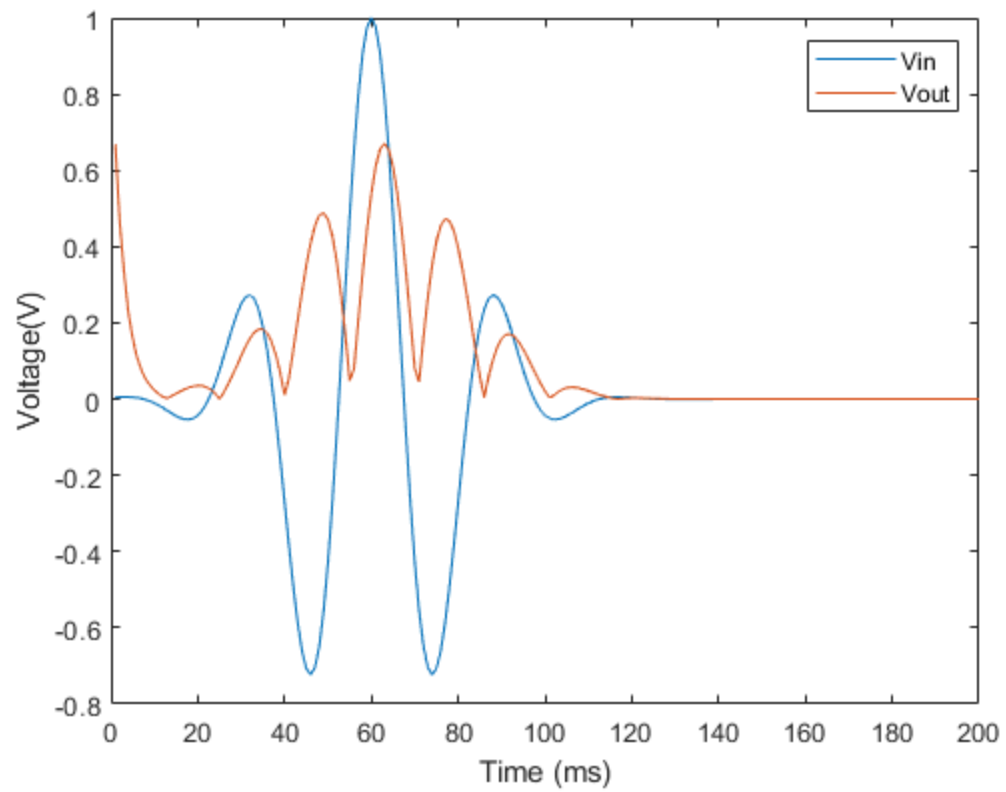

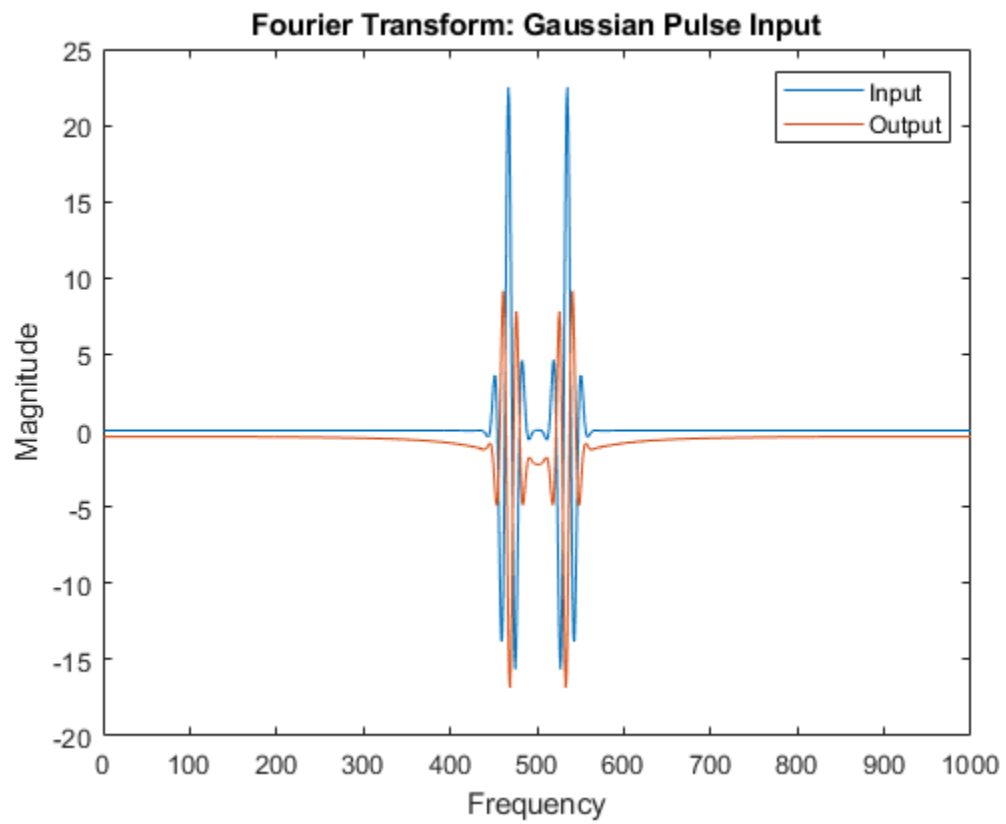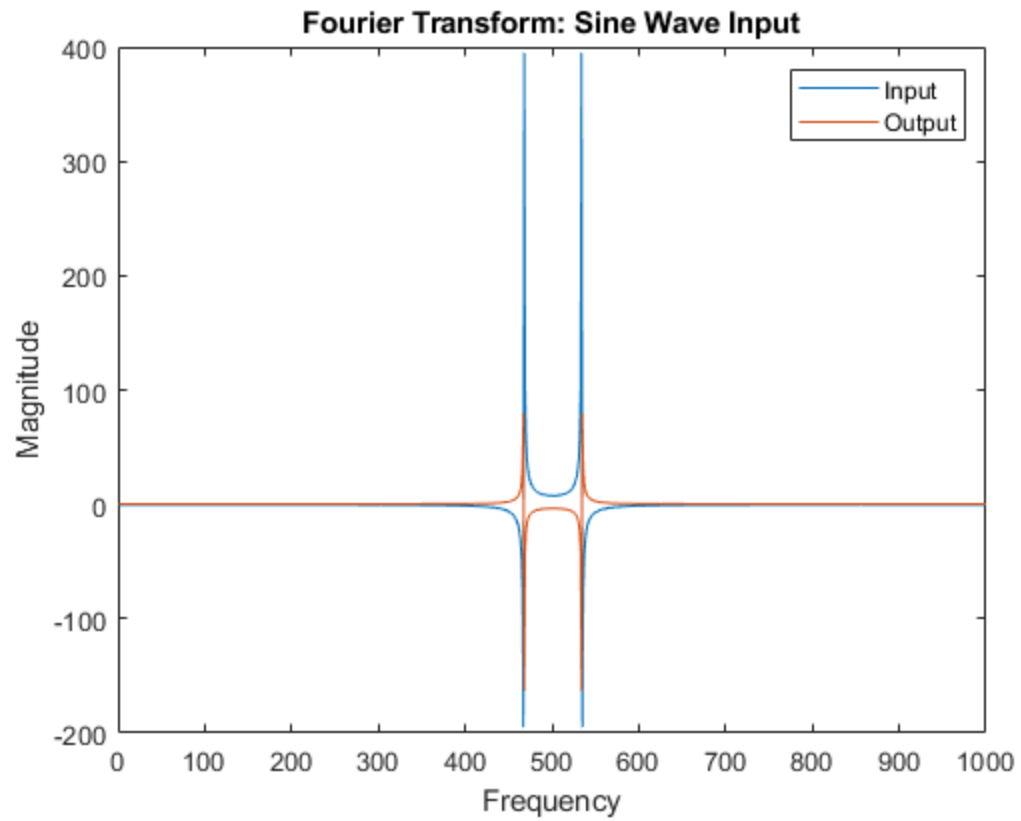

Question 5

```
Cn = 0.00001
In = 0,001 % initial I0
G = [
    1    0    0    0    0    0    0;
   -1/R2  (1/R1)+(1/R2)  -1    0    0    0    0;
    0    1    0   -1    0    0    0;
    0    0   -1   1/R3   In    0    0;
    0    0    0    0  -alpha    1    0;
    0    0    0   1/R3   -1    0    0;
    0    0    0    0    0  -1/R4  (1/R4)+(1/Ro)];

C_Mat = [
    0    0    0    0    0    0    0;
   -C    C    0    0    0    0    0;
    0    0   -L    0    0    0    0;
    0    0    0   Cn    0    0    0;
    0    0    0    0    0    0    0;
    0    0    0    0    0    0    0;
    0    0    0    0    0    0    0];

% V = [V2; V1; I1; V3; I3; V4; Vo]

for time = dt:dt:simulation_time

    input_C(1,time) = (exp(-2*log(2)*(time-60).^2/
(30)^2)).*cos(-2*pi*f*(time-60));

    F=[input_C(1,time); 0; 0; 0; 0; 0; 0];

    Vout = (G +C)\ (C.*Vpre) + F;
    Vout3_store(1,time) = Vout(7);

    Vpre = Vout;
    In = normrnd(0.001,0.01);
end

Time = linspace(dt,simulation_time,simulation_time);

figure(12)
plot(Time,input_C)
hold on;
plot(Time,abs(Vout3_store))
xlim([0 200])
% ylim([-1.1 1.1])
title('Vout and Vin w/ Cn and random In')
xlabel('Time (ms)')
ylabel('Voltage(V)')
hold off
legend('Vin','Vout')

figure(13)
```

```

plot(Time,fft(Vout3_store))
% ylim([-1.1 1.1])
title('Fourier Transform of Output')
xlabel('Time (ms)')
ylabel('Voltage(V)')
hold off
dt = 100;
for time = 1:dt:simulation_time

    input_C(1,time) = (exp(-2*log(2)*(time-60).^2/
(30)^2)).*cos(-2*pi*f*(time-60));

    F =[input_C(1,time); 0; 0; 0; 0; 0; 0];

    Vout = (G +C)\ (C.*Vpre) + F;
    Vout3_store(1,time) = Vout(7);

    Vpre = Vout;
    In = normrnd(0.001,0.01);
end

Time = linspace(dt,simulation_time,simulation_time);

figure(14)
plot(Time,input_C)
hold on;
plot(Time,abs(Vout3_store))
    xlim([0 200])
% ylim([-1.1 1.1])
title('Vout and Vin w/ Cn and random In (1/100 time step)')
xlabel('Time (ms)')
ylabel('Voltage(V)')
hold off
legend('Vin','Vout')

figure(15)
plot(Time,fft(Vout3_store))
% ylim([-1.1 1.1])
title('Fourier Transform of Output (1/100 time step)')
xlabel('Time (ms)')
ylabel('Voltage(V)')
hold off
dt = 10;
for time = 1:dt:simulation_time

    input_C(1,time) = (exp(-2*log(2)*(time-60).^2/
(30)^2)).*cos(-2*pi*f*(time-60));

    F =[input_C(1,time); 0; 0; 0; 0; 0; 0];

    Vout = (G +C)\ (C.*Vpre) + F;
    Vout3_store(1,time) = Vout(7);

    Vpre = Vout;

```

```

        In = normrnd(0.001,0.01);
    end

    Time = linspace(dt,simulation_time,simulation_time);

    figure(16)
    plot(Time,input_C)
    hold on;
    plot(Time,abs(Vout3_store))
        xlim([0 200])
        % ylim([-1.1 1.1])
    title('Vout and Vin w/ Cn and random In (1/10s step)')
    xlabel('Time (ms)')
    ylabel('Voltage(V)')
    hold off
    legend('Vin','Vout')

    figure(17)
    plot(Time,fft(Vout3_store))
        % ylim([-1.1 1.1])
    title('Fourier Transform of Output (1/10s Time step)')
    xlabel('Time (ms)')
    ylabel('Voltage(V)')
    hold off

    Cn =

        1.0000e-05

    In =



        0



    ans =



        1

    Warning: Imaginary parts of complex X and/or Y arguments ignored
    Warning: Imaginary parts of complex X and/or Y arguments ignored
    Warning: Imaginary parts of complex X and/or Y arguments ignored

```

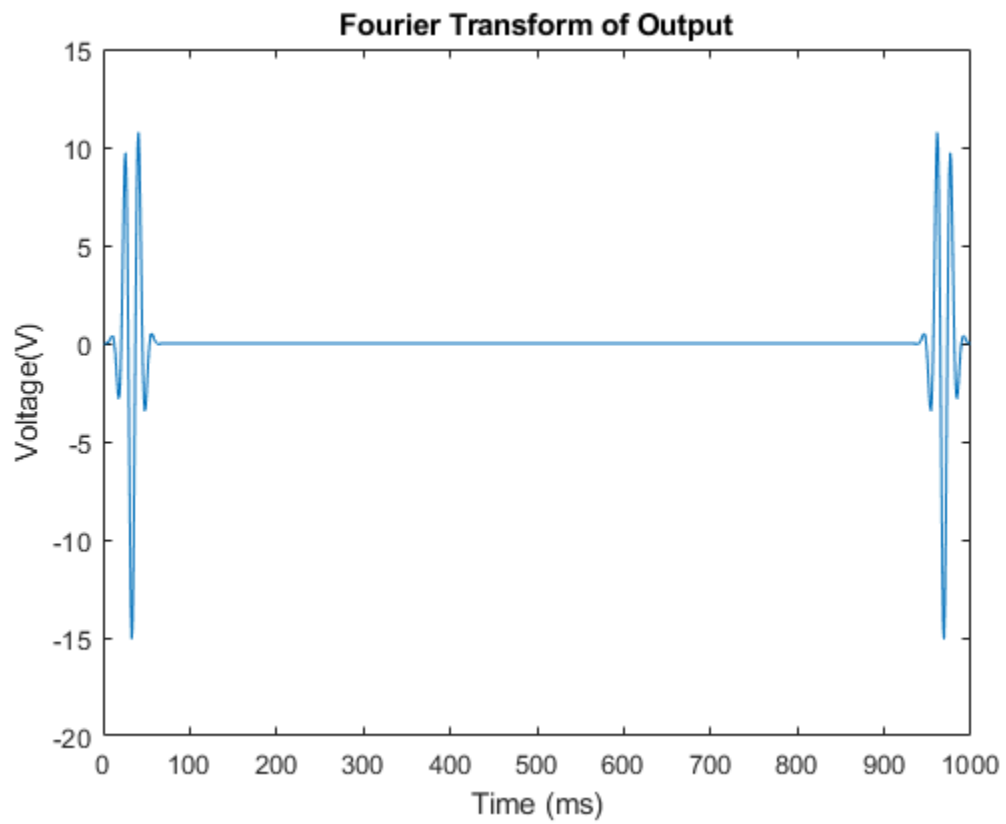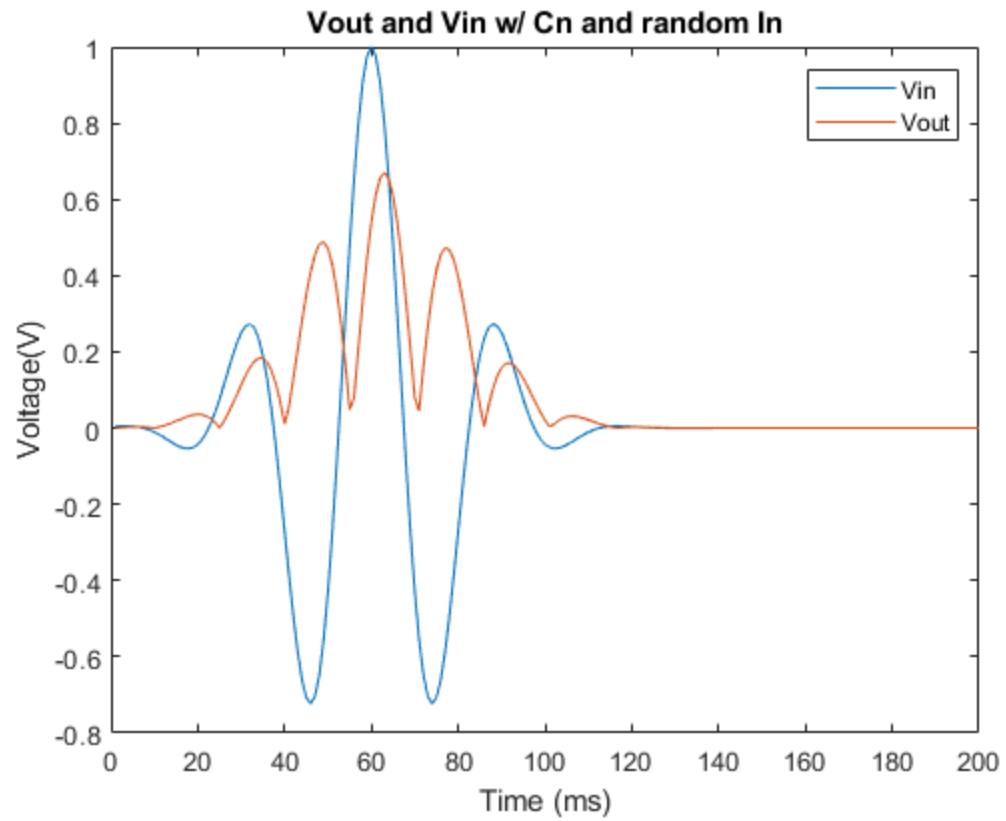

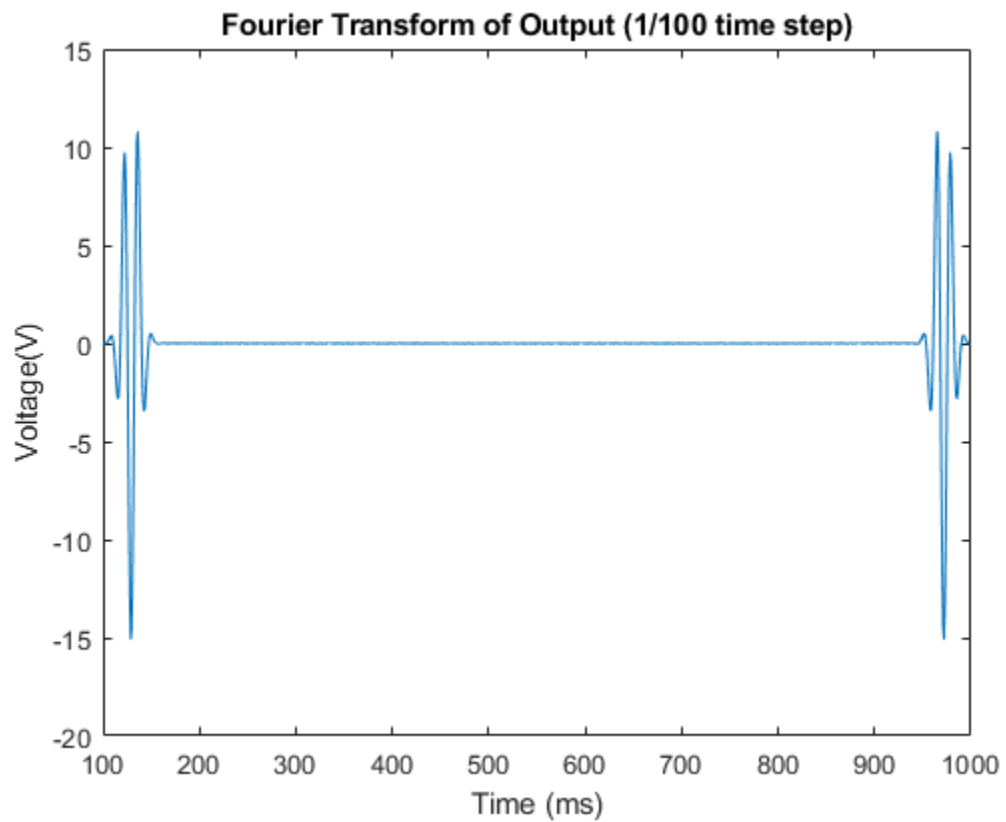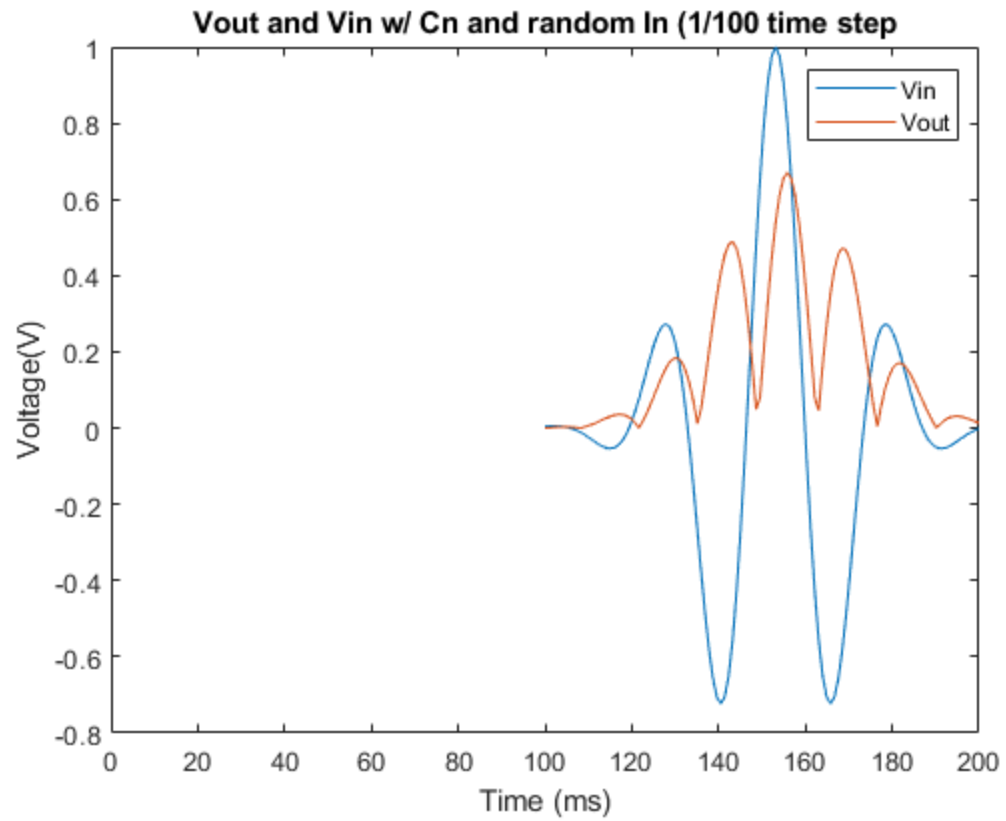

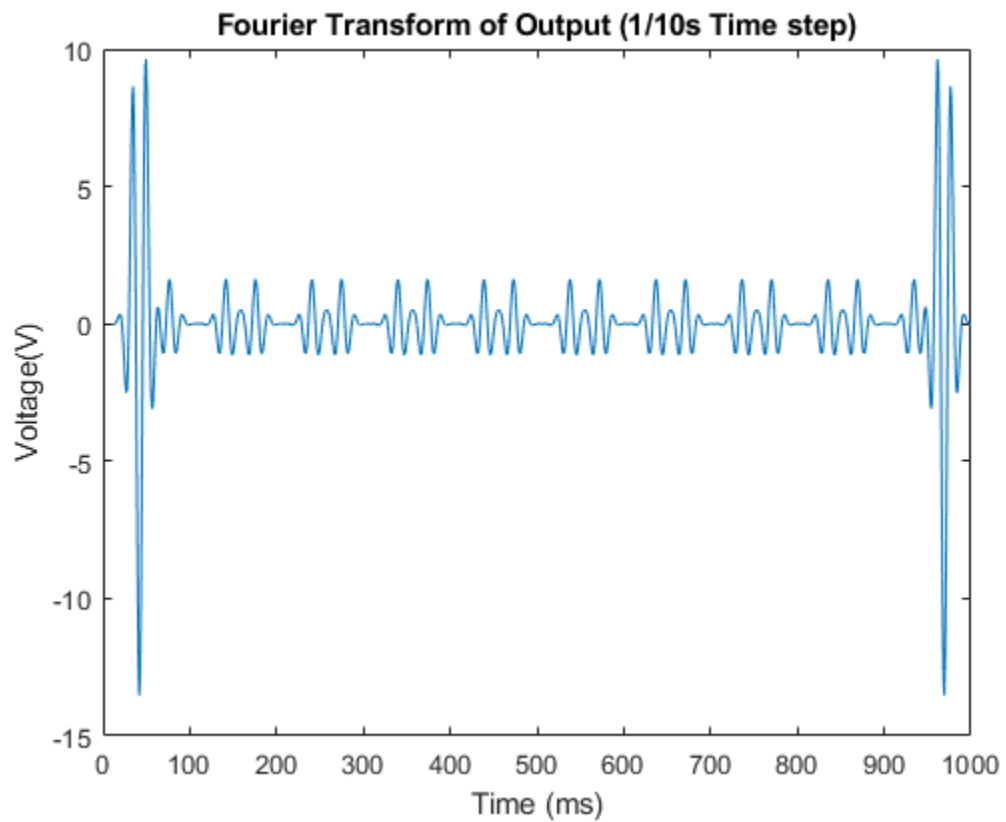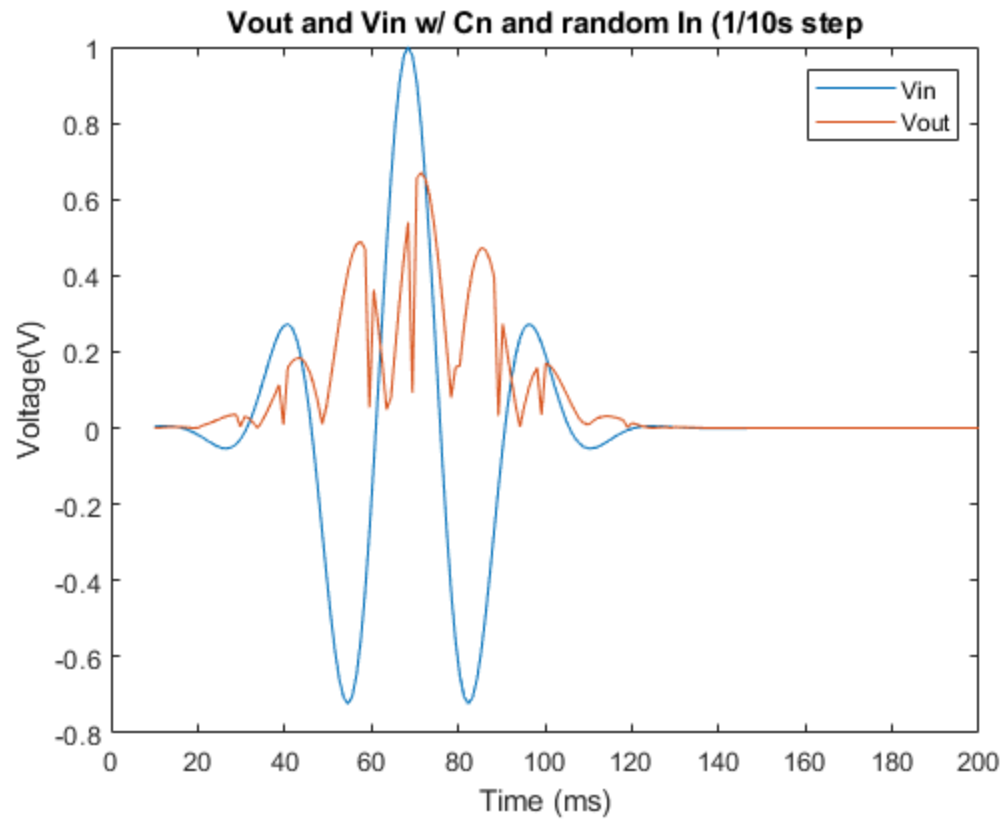

Published with MATLAB® R2019b